

# Digital Logic

COMP370  
Introduction to Computer Architecture

## Logic Simplification

- It is frequently possible to simplify a logical expression. This makes it easier to understand and requires fewer gates to implement.
- There are several simplification techniques including Boolean algebra and Karnaugh maps.

## Boolean Simplification Example

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

$$F = A'B'C' + A'B'C + A'BC' + ABC'$$

## Applying Boolean Identities

$F = A'B'C' + A'B'C + A'BC' + ABC'$	Rule
$F = A'B'(C' + C) + A'BC' + ABC'$	Distribution
$F = A'B'(1) + A'BC' + ABC'$	Complement
$F = A'B' + A'BC' + ABC'$	Identity
$F = A'B' + BC'(A' + A)$	Distribution
$F = A'B' + BC'(1)$	Complement
$F = A'B' + BC'$	Identity

## Karnaugh maps

- Another way to simplify Boolean expressions is to use Karnaugh maps
- Karnaugh maps use a visual table to help identify parts of a Boolean expression that can be combined.
- It only works well for Boolean expressions that have 3 or 4 input variables.

## 3 Variable Karnaugh Map

- Create a table of the 8 possible input combinations in a specific (*gray code*) order.

	B'C'	B'C	BC	BC'
A'	0	1	3	2
A	4	5	7	6

The numbers shown in the table are the decimal value of the three input bits when considered as a binary number.

## Karnaugh Example

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Copy the output values into the Karnaugh map.

	B'C'	B'C	BC	BC'
A'	1	1	0	1
A	0	0	0	1

## Grouping Ones

- To simplify the equation, you want to group the squares with a "1" into as large a group as you can.
- Imagine that the table wraps around both sides and top and bottom. It is a *Torus*
- You want to create big groups rather than small groups.
- A single square can be in multiple groups if it helps make big groups.

## Grouping Ones

- To simplify the equation, you want to group the squares with a "1" into as large a group as you can.

	B'C'	B'C	BC	BC'
A'	1	1	0	1
A	0	0	0	1

$$F = A'B' + BC'$$

## Group of 8

- If every square is a "1" then the function is always true.

	B'C'	B'C	BC	BC'
A'	1	1	1	1
A	1	1	1	1

$$F = 1$$

## Groups of 4

- A group of 4 indicates a single variable.

	B'C'	B'C	BC	BC'
A'	1	1	1	1
A	1	1	1	1

$$F = A' \quad F = A$$

## Groups of 4

- A group of 4 indicates a single variable.

	B'C'	B'C	BC	BC'
A'	1	1	1	1
A	1	1	1	1

$$F = B' \quad F = B$$

## Groups of 4

- A group of 4 indicates a single variable.

	B'C'	B'C	BC	BC'
A'	1	1	1	1
A	1	1	1	1

$$F = C' \quad F = C$$

## Mapping Column to Variable

- Each column represents a pair of variables.

	B'C'	B'C	BC	BC'
A'	1	1	0	1
A	0	0	0	1

$\swarrow$  B'       $\swarrow$  B  
 $\nwarrow$  C'       $\nearrow$  C  
 $\nwarrow$  C'       $\nearrow$  C

## Groups of 2

- A group of 2 indicates a pair of variables.

	B'C'	B'C	BC	BC'
A'	1	1	1	1
A	1	1	1	1

$$F = B'C' \quad F = B'C \quad F = BC \quad F = BC'$$

## Groups of 2

- A group of 2 indicates a pair of variables.

	B'C'	B'C	BC	BC'
A'	1	1	1	1
A	1	1	1	1

$$F = A'B' \quad F = AB' \quad F = A'B \quad F = AB$$

## Groups of 2

- A group of 2 indicates a pair of variables.

	B'C'	B'C	BC	BC'
A'	1	1	1	1
A	1	1	1	1

$$F = A'C' \quad F = A'C \quad F = AC' \quad F = AC$$

## Groups of One

- If a single square in the Karnaugh map cannot be combined with any other then it is expressed by all three variables.

	B'C'	B'C	BC	BC'
A'	0	1	0	0
A	0	0	0	1

$$F = A'B'C + ABC'$$

## Karnaugh Example

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Copy the output values into the Karnaugh map.

	B'C'	B'C	BC	BC'
A'	1	1	0	0
A	0	1	0	0

## Karnaugh Example

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Copy the output values into the Karnaugh map.

	B'C'	B'C	BC	BC'
A'	1	1	0	0
A	0	1	0	0

$$F = A'B' + B'C$$

## Simplify this Truth Table

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

	B'C'	B'C	BC	BC'
A'				
A				

## Simplified Truth Table

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

	B'C'	B'C	BC	BC'
A'	0	1	1	1
A	0	0	1	1

$$F = B + A'C$$

## Simplify Another Truth Table

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

	B'C'	B'C	BC	BC'
A'				
A				

## Another Simplified Truth Table

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

	B'C'	B'C	BC	BC'
A'	1	1	0	1
A	0	1	0	0

$$F = A'C' + B'C$$

## Simplify the Boolean Equation

$$F = A'B'C' + A'BC + ABC$$

	B'C'	B'C	BC	BC'
A'				
A				

## Simplified Boolean Equation

$$F = A'B'C' + A'BC + ABC$$

	B'C'	B'C	BC	BC'
A'	1	0	1	0
A	0	0	1	0

$$F = A'B'C' + BC$$

## Ignored Input Combinations

- Sometimes the logical system will not have certain input combinations.
- It may not matter what the output is for input combinations that will not occur.
- Karnaugh map squares can be marked with a "d" for Don't care.
- A "don't care" may be included to make a big group, but do not have to be included.

## Truth Table with "Don't Care"

A	B	C	F
0	0	0	d
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	d
1	1	1	0

Note that one "d" was included to make a big group while the other was ignored.

	B'C'	B'C	BC	BC'
A'	d	1	0	0
A	1	1	0	d

$$F = B'$$

## 4 Input Karnaugh maps

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

Note the Gray Code order both horizontally and vertically.  
The top and bottom are adjacent as well as the left and right.

## Single Variable Group of 8

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

$$F = C' \quad F = C$$

## Single Variable Group of 8

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

$$F = A' \quad F = A$$

## Single Variable Group of 8

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

$$F = B' \quad F = B$$



## Single Variable Group of 8

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

$$F = D' \quad F = D$$

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Three Variable Pairs

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

### Three Variable Pairs

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

### Three Variable Pairs

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

### Three Variable Pairs

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

### 4 Input Example


$$F = AB + C'D$$

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

	$C'D'$	$C'D$	$CD$	$CD'$
$A'B'$	0	1	0	0
$A'B$	0	1	0	0
$AB$	1	1	1	1
$AB'$	0	1	0	0
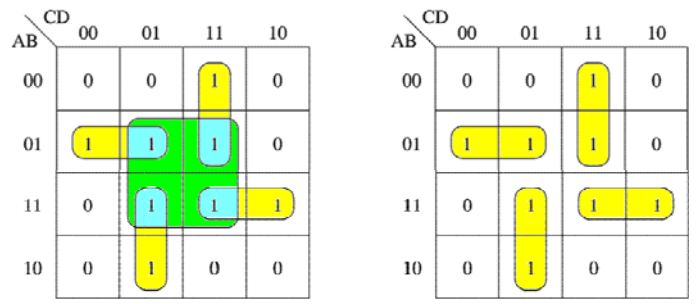
### Unnecessary Groups

- Avoid groups that do not contain any squares that are not already in a group.



(a) Nonminimal simplification


(b) Minimal simplification

### Karnaugh Map Process

- Fill the Karnaugh map with 0's, 1's and d's
- Group the 1's into as big as group as possible. Include d's only if necessary.
- Do not include 0's in the groups.
- Write the Boolean expression for each group with the groups ORed together.

### 7 Segment Display

A	B	C	D	a	b	c	d	e	f	g	
0	0	0	0	1	1	1	1	1	1	0	0
0	0	0	1	0	1	1	0	0	0	0	1
0	0	1	0	1	1	0	1	1	0	1	2
0	0	1	1	1	1	1	1	0	0	1	3
0	1	0	0	0	1	1	0	0	1	1	4
0	1	0	1	1	0	1	1	0	1	1	5
0	1	1	0	0	0	1	1	1	1	1	6
0	1	1	1	1	1	1	0	0	0	0	7
1	0	0	0	1	1	1	1	1	1	1	8
1	0	0	1	1	1	1	0	0	1	1	9

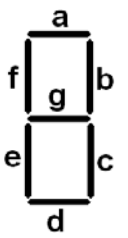

Inputs 0xA – 0xF should not occur, so the output is "don't care"

### Segment "b" of Display

A	B	C	D	b
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B	1	0	1	0
AB	d	d	d	d
AB'	1	1	d	d

### Segment "b" of Display

A	B	C	D	b
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1

	C'D'	C'D	CD	CD'
A'B'	1	1	1	1
A'B	1	0	1	0
AB	d	d	d	d
AB'	1	1	d	d

seg b = B' + C'D' + CD

### Segment "a" of Display

A	B	C	D	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1

	C'D'	C'D	CD	CD'
A'B'	1	0	1	1
A'B	0	1	1	0
AB	d	d	d	d
AB'	1	1	d	d

### Segment "a" of Display

A	B	C	D	a
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1

	C'D'	C'D	CD	CD'
A'B'	1	0	1	1
A'B	0	1	1	0
AB	d	d	d	d
AB'	1	1	d	d

sega=B'D' + AD + CD + AB'

### Simplify Segment "f"

A	B	C	D	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1

	C'D'	C'D	CD	CD'
A'B'				
A'B				
AB				
AB'				

### Simple Segment "f"

A	B	C	D	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1

	C'D'	C'D	CD	CD'
A'B'	1	0	0	0
A'B	1	1	0	1
AB	d	d	d	d
AB'	1	1	d	d

$$F = A + C'D' + BC' + BD'$$

### Simplify Segment "d"

A	B	C	D	d
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0

	C'D'	C'D	CD	CD'
A'B'				
A'B				
AB				
AB'				

### Simplified Segment "d"

A	B	C	D	d
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0

	C'D'	C'D	CD	CD'
A'B'	1	0	1	1
A'B	0	1	0	1
AB	d	d	d	d
AB'	1	0	d	d

$$F = B'D' + B'C + CD' + BC'D$$

### Karnaugh Maps for Programming

```

if (((S <6)&&(L>10)) ||
    ((S>=6)&&(N==G)&&(L>10)) ||
    ((N==G)&&(L<=10)) ||
    ((S>=6)&&(N==G)) ||
    ((S>=6)&&(N!=G)&&(L>10)) ) {

    print "OK";

}
    
```

### Fill Table with IF Clauses

**S** is ( $S \geq 6$ )    **L** is ( $L > 10$ )    **N** is ( $N == G$ )

**S'** is ( $S < 6$ )    **L'** is ( $L \leq 10$ )    **N'** is ( $N \neq G$ )

	<b>S'N'</b>	<b>S'N</b>	<b>SN</b>	<b>SN'</b>
<b>L'</b>	0	1	1	0
<b>L</b>	1	1	1	1

**if** ((**N==G**) || (**L>10**))