

VLSI

COMP370
Intro to Computer Architecture

Layers

- Applications
- Middleware – other CS classes
- High level languages
- Machine Language
- Microcode
- Logic circuits
- Gates
- Transistors
- Silicon structures

Layers

- Applications
- Middleware
- High level languages
- Machine Language – COMP375
- Microcode
- Logic circuits
- Gates
- Transistors
- Silicon structures

Layers

- Applications
- Middleware
- High level languages
- Machine Language
- Microcode
- Logic circuits – this semester
- Gates
- Transistors
- Silicon structures

Layers

- Applications
- Middleware
- High level languages
- Machine Language
- Microcode
- Logic circuits
- **Gates – Earlier with more to come**
- Transistors
- Silicon structures

Layers

- Applications
- Middleware
- High level languages
- Machine Language
- Microcode
- Logic circuits
- Gates
- **Transistors - Today**
- **Silicon structures**


Periodic Table of Elements

The image shows a standard periodic table of elements. It includes group labels (1a through 8, 9, 10, 11, 12, 13, 14, 15, 16, 17, 18, and 0) and period labels (1 through 7). The elements are arranged in rows and columns based on their atomic number and chemical properties. The lanthanides and actinides are shown at the bottom of the table.

Silicon


- Silicon has a valance of 4 and is in the middle of its row in the periodic table.
- Pure Silicon is a very poor conductor.
- Phosphorus has one more electron than Silicon. It is a **N** type dopant.
- Boron has one less electron than Silicon. It is an **P** type dopant.
- Adding just one part per million or less of a **P** dopant to silicon gives it extra electrons making it a good conductor.

n-channel MOS transistor

 


- Metal** good conductor for gates
- lightly P-doped silicon** normally poor conductor
- heavily N-doped silicon** good conductor
- Silicon Dioxide (glass)** insulator

NPN Transistor Operation

 


The low concentration P type silicon is a poor conductor. Therefore very little current flows from the source to the gate.

Transistor Operation

 

When positive voltage is applied to the gate, electrons are attracted to the gate. The presence of electrons allows current to flow between the source and drain.

PNP Transistor

 

Infusing a lot of N dopant in an area makes a well of N doped silicon. A PNP transistor can be built in the well.


Complementary Operation

- **NPN** transistors conduct electricity between the source and drain when current is applied to the gate.
- **PNP** transistors conduct electricity between the source and drain when **no** current is applied to the gate. They stop conducting when current is applied to the gate.

CMOS


- **C**omplementary **M**etal **O**xide **S**emiconductor is a design technique using both NPN and PNP transistors.
- PNP transistors are used to connect the power to the output.
- NPN transistors are used to connect the ground to the output.
- The PNP and NPN circuits are exact logical inverses.

NPN Transistor Stick Diagram


 


Conducts when the gate has current.


PNP Transistor Stick Diagram

 

 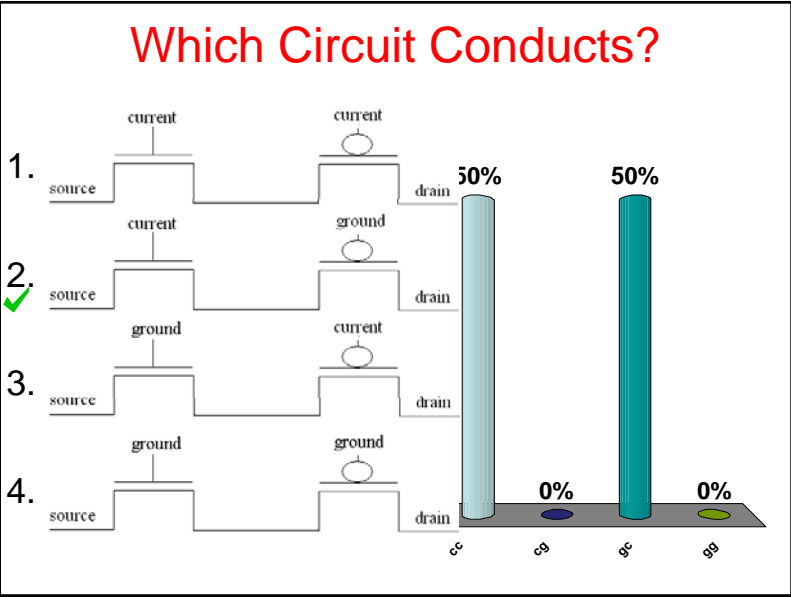Conducts when the gate does not have current.



 - ### Capacitance
- Capacitance is a circuit's ability to hold a charge.
 - Greater capacitance increases the time required for a circuit to change voltage.
 - Increasing the width of the transistor elements increases the capacitance.




Very Large Scale Integration

- Transistors and the circuitry connecting them is built on a chip of silicon using **photolithography**.
- Millions of transistors can be manufactured on a single chip.


VLSI Manufacturing

- Part 1
<http://www.youtube.com/watch?v=tdkJ5Nn8oaM&feature=related>
- Part 2
<http://www.youtube.com/watch?v=UwT-HPCR5Gg&feature=related>
- Part 3
<http://www.youtube.com/watch?v=A70cW9jOZqc&feature=related>


Photoresist

 



Photolithography Etching

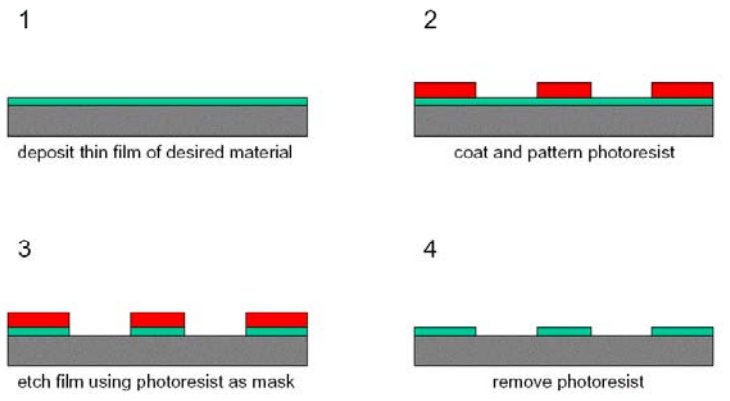

Photolithography Lift-off

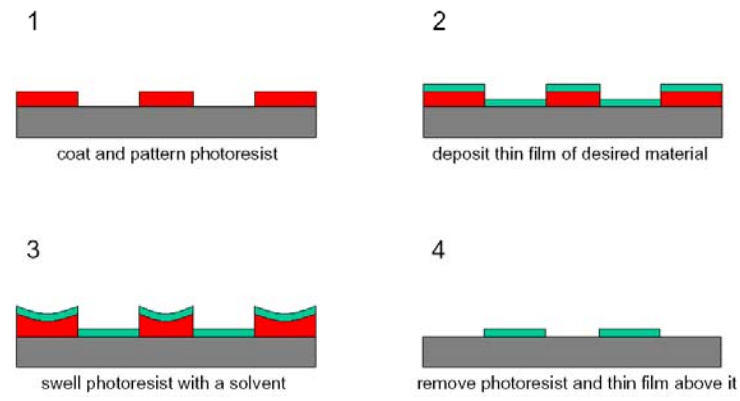


Projection Techniques

  

What Does Photoresist Do?


1. Interconnects the circuits
- ★ 2. Shields the silicon from chemicals
3. It is a dopant
4. Dissolves silicon

Logic Gate Components

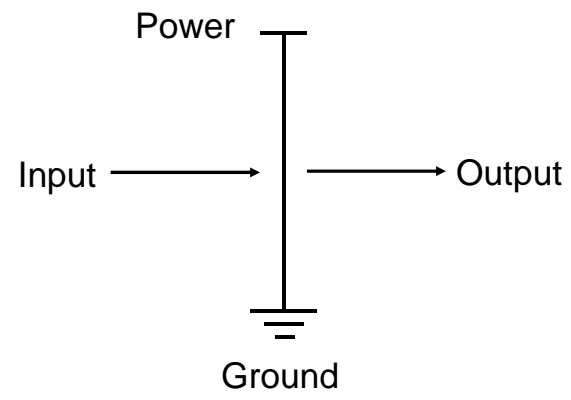

Not Gate

 
- When the input is 1 (current) the upper PNP transistor does not conduct. Power cannot flow to the output
- The lower NPN transistor does conduct. The output is connected to ground.
- When the input is 0 (no current) the upper PNP transistor can conduct power to the output.
- The lower NPN transistor does not connect the output to ground.




- When either A or B is 0, the output is connected to power.
- When both A and B are one, the output is connected to ground.

A	B	output
0	0	1
0	1	1
1	0	1
1	1	0

NAND Gate

 


CMOS NAND transistors

 

- When A & B are 0, the output is connected to power.
- When either A or B are one, the output is connected to ground.

A	B	output
0	0	1
0	1	0
1	0	0
1	1	0

 


Shorts


- It is important that no combination of inputs connects both the power and ground to the output. Power would flow from the power source to the ground creating a short and melting the chip.
- The output should always be connected to either the power or the ground. Otherwise the output will "float".

Static RAM Cell

 - Draw the below gate diagram using only transistors.



CMOS Static RAM Bit

 

More Complex Example

- Consider the carry out equation for a one bit adder

$$\overline{Cout} = AB + BC + AC$$

- The complement is

$$Cout = (\overline{A+B})(\overline{B+C})(\overline{A+C})$$

CMOS Carry Circuit

