


# Digital Logic


COMP375 Computer Architecture  
and Organization


## Types of Digital Logic

- **Combinational Logic** – Digital circuits that have no memory. The same inputs always produce the same output.
- **Sequential Logic** – Logic elements with memory whose output depends on the input and the current contents of the memory.


## Logic Gates


AND \* 

OR + 

NOT  $\bar{X}$  

## Negative Logic Gates

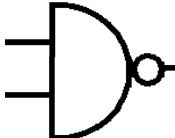NAND 

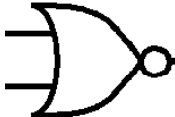NOR 

## Boolean Laws

Identity	$X + 0 = X$ and $X * 1 = X$
One	$X + 1 = 1$
Zero	$X * 0 = 0$
Inverse	$\bar{X} + X = 1$ and $\bar{X} * X = 0$
Reflexive	$X + X = X$ and $X * X = X$
Commutative	$X + Y = Y + X$ and $X * Y = Y * X$
Associative	$X + (Y + Z) = (X + Y) + Z$ $X * (Y * Z) = (X * Y) * Z$

## Boolean Laws

Distributive	$X * (Y + Z) = (X * Y) + (X * Z)$ $X + (Y * Z) = (X + Y) * (X + Z)$
DeMorgan's	$X + Y = \overline{\bar{X} * \bar{Y}}$ $X * Y = \overline{\bar{X} + \bar{Y}}$

## Sum of Product Form

Sum of Product	$(A * B) + (C * D)$
Product of Sums	$(A + B) * (C + D)$

## Truth Table to Function


- A sum of products solution can be written by ORing the lines of the truth table that are true.

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C}$$

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

## Programmable Logic Array

- PLAs implement the sum of products

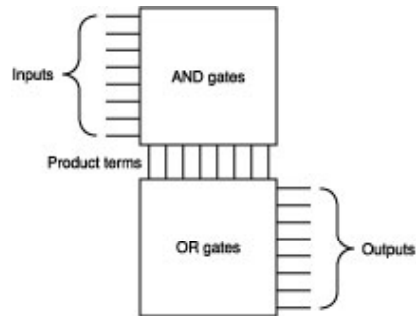

## Sequential Logic


- Some logic circuits have memory that determines the future outcome of the circuit.
- Flip-flops are a simple sequential logic elements.



## SR Flip-Flops

- An SR flip-flop can be constructed from two NOR gates


S	R	Action
0	0	Keep state
0	1	$Q = 0$
1	0	$Q = 1$
1	1	Restricted combination

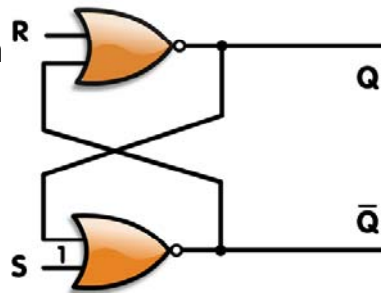

## D Flip-Flop

- A D flip-flop has only one data input plus enable, C

C	D	$Q_{next}$	Comment
0	X	$Q_{prev}$	No change
1	0	0	Reset
1	1	1	Set

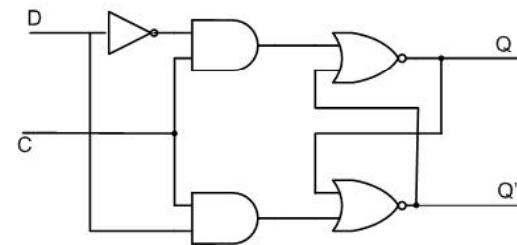

## Logic Simplification

- It is frequently possible to simplify a logical expression. This makes it easier to understand and requires fewer gates to implement.
- There are several simplification techniques including Boolean algebra and Karnaugh maps.

## Karnough maps

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Single Variable Group of 8

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Single Variable Group of 8

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Single Variable Group of 8

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Single Variable Group of 8

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Two Variable Group of 4

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Three Variable Pairs

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Three Variable Pairs

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Three Variable Pairs

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Three Variable Pairs

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0000	0001	0011	0010
$\bar{A}B$	0100	0101	0111	0110
$AB$	1100	1101	1111	1110
$A\bar{B}$	1000	1001	1011	1010

## Example 1 bit Subtraction

$$\text{Diff} = X - Y$$

Bin	X	Y	Dif	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	1

## Subtraction Karnough Maps

	$\bar{X}\bar{Y}$	$X\bar{Y}$	$XY$	$\bar{X}Y$
$\bar{\text{Bin}}$	0	1	0	1
Bin	1	0	1	0

$$\text{Dif} = \bar{X}\bar{Y}\text{Bin} + X\bar{Y}\bar{\text{Bin}} + XY\text{Bin} + \bar{X}Y\bar{\text{Bin}}$$

## Subtraction Karnough Maps

	$\bar{X}\bar{Y}$	$\bar{X}Y$	$XY$	$X\bar{Y}$
$\bar{\text{Bin}}$	0	1	0	0
Bin	1	1	1	0

$$\text{Bout} = \bar{X}\text{Bin} + \bar{X}Y + Y\text{Bin}$$